

Using the node-voltage method, calculate the four resistor voltages.

$V_{R1} =$ _____

$V_{R2} =$ _____

$V_{R3} =$ _____

$V_{R4} =$ _____

