

Use the mesh-current method to find the currents in  $R_1$ ,  $R_3$ , and  $R_5$  in the circuit shown at right.

$i_{R1} =$  \_\_\_\_\_

$i_{R3} =$  \_\_\_\_\_

$i_{R5} =$  \_\_\_\_\_

