

Use the method of superposition to find the values of  $v_{R2}$  and  $v_{R6}$  in the circuit at right.

$v_{R2} =$  \_\_\_\_\_

$v_{R6} =$  \_\_\_\_\_

