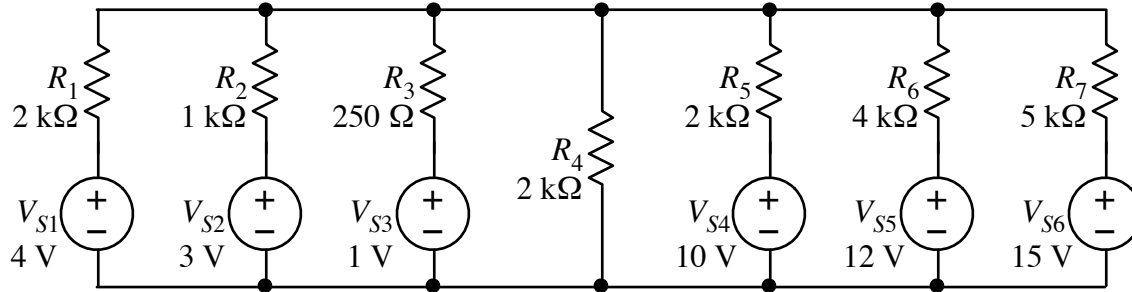


For the circuit shown below, find the current flowing in each of the resistors. Use the node-voltage method.



$i_{R1} =$ _____ ; $i_{R2} =$ _____ ; $i_{R3} =$ _____ ; $i_{R4} =$ _____

$i_{R5} =$ _____ ; $i_{R6} =$ _____ ; $i_{R7} =$ _____