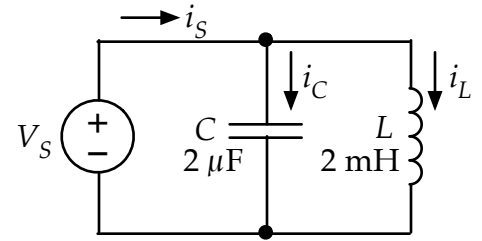


In the circuit shown at right, the voltage source is sinusoidal with

$$V_S(t) = V_m \cos(\omega t),$$

where $V_m = 5 \text{ V}$ and $\omega = 2500 \text{ rad/s}$. Write the expression for the total current flowing through the source. Then repeat for $\omega = 5000 \text{ rad/s}$.




$$i_S (\omega = 2500 \text{ rad/s}) = \underline{\hspace{10cm}}$$

$$i_S (\omega = 5000 \text{ rad/s}) = \underline{\hspace{10cm}}$$

In the circuit shown at right, the current source is sinusoidal with

$$I_S(t) = I_m \sin(\omega t),$$

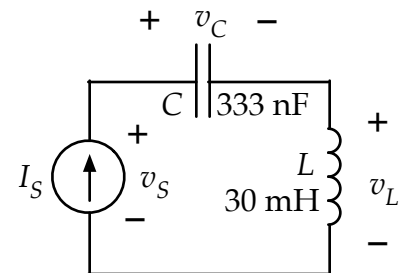where $I_m = 20 \text{ mA}$ and $\omega = 20,000 \text{ rad/s}$. Write the expression for the total voltage across the source. Then repeat for $\omega = 10,000 \text{ rad/s}$.



$$v_S (\omega = 20,000 \text{ rad/s}) = \underline{\hspace{10cm}}$$

$$v_S (\omega = 10,000 \text{ rad/s}) = \underline{\hspace{10cm}}$$