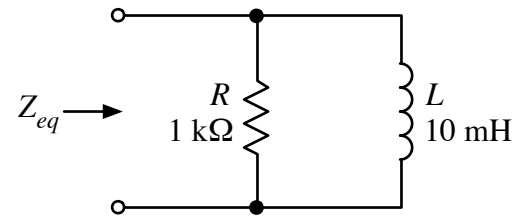


- a. For the  $RL$  parallel combination shown at right, what is the angular frequency at which the *magnitude* of the equivalent impedance be equal to  $500 \Omega$ ?



$$\omega = \underline{\hspace{10cm}}$$

- b. What is the phase angle of the impedance at the frequency calculated in part (a) above?

$$\theta = \underline{\hspace{10cm}}$$

- c. At what angular frequency is the phase angle of  $Z_{eq}$  equal to  $+45^\circ$ ?

$$\omega = \underline{\hspace{10cm}}$$

- d. What is the magnitude of the impedance at the frequency calculated in part (c) above?

$$|Z_{eq}| = \underline{\hspace{10cm}}$$

- e. What is the magnitude of the impedance as  $\omega \rightarrow 0$ ?

$$|Z_{eq}| = \underline{\hspace{10cm}}$$

- f. What is the magnitude of the impedance as  $\omega \rightarrow \infty$ ?

$$|Z_{eq}| = \underline{\hspace{10cm}}$$