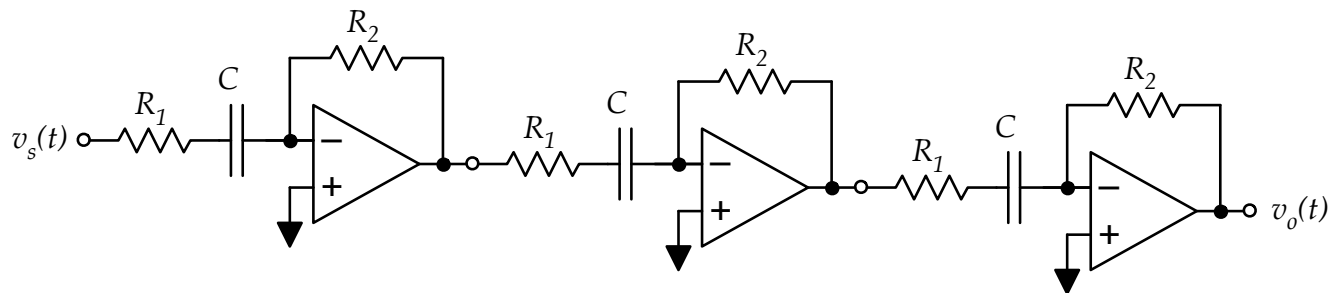


Calculate the transfer function for the circuit shown below. Express your result as a ratio of two polynomials. The op-amps are ideal.



$T(s) = V_o(s)/V_s(s) =$  \_\_\_\_\_.