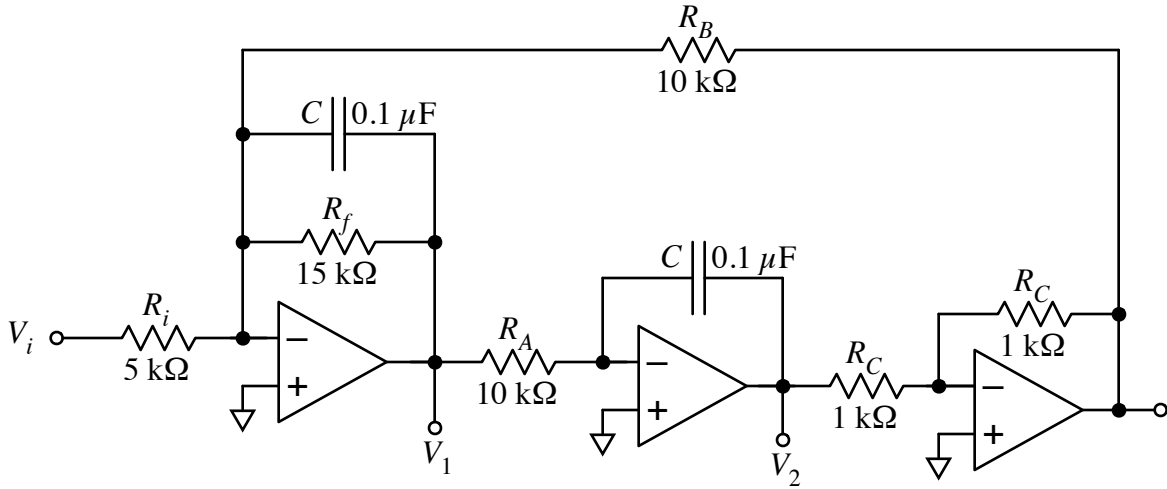


Below is another version of a two-integrator loop, similar to the KHN, but slightly simpler. It produces two of the standard 2nd-order filter functions. It is known as the Tow-Thomas biquad.



Show that $T_1(s) = V_1/V_i$ is a bandpass function: $T_1(s) = -\frac{R_f}{R_i} \cdot \frac{s\left(\frac{1}{R_f C}\right)}{s^2 + s\left(\frac{1}{R_f C}\right) + \frac{1}{R_A R_B C^2}}$.

For the component values given in the circuit, determine

$f_o =$ _____ ; $Q_P =$ _____ ; $G_o =$ _____

Then find the other transfer function $T_2(s) = V_2/V_i$.

$T_2(s) =$ _____