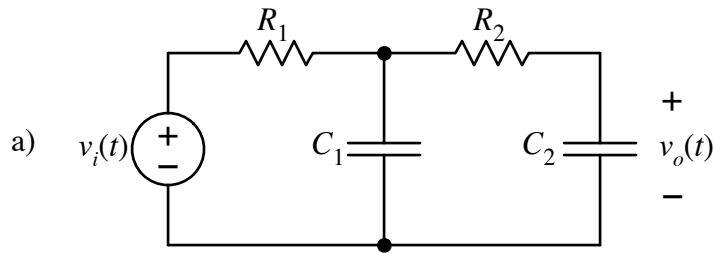
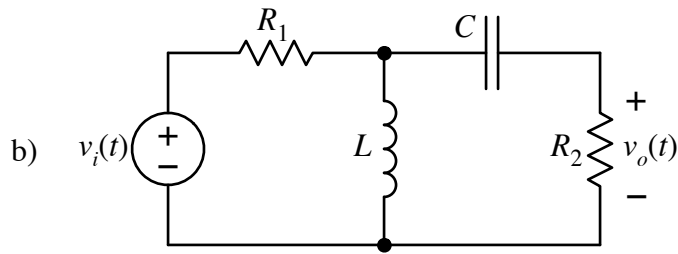


Find the frequency-domain expression for the requested quantities in the two circuits shown below. The sources are not specified — include the source in your answers as simply $V_i(s)$.



$V_o(s) =$ _____



$V_o(s) =$ _____