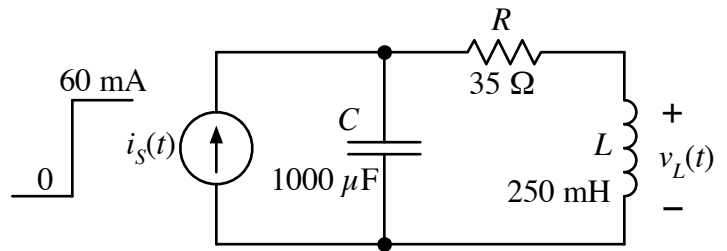


The current source in the circuit at right steps abruptly from 0 to 60 mA at  $t = 0$ .



- a) Find the frequency-domain expression for the inductor voltage. Simplify the expression so that it is in the form of ratio of two polynomials.

$$V_L(s) = \underline{\hspace{15em}}$$

- b) Find the corresponding time-domain expression for the inductor voltage.

$$v_L(t) = \underline{\hspace{15em}}$$