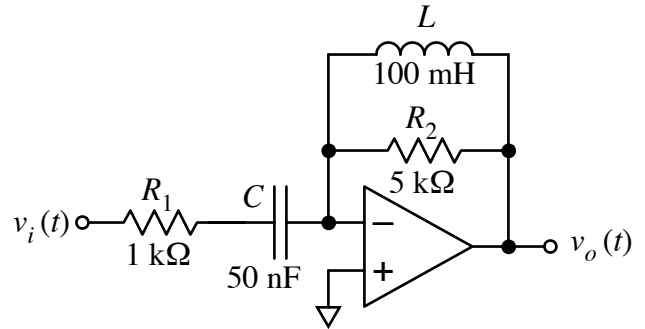



For each of the circuits below, calculate the transfer function — express the function in symbols (i.e. using  $R_s$ ,  $L_s$ , and  $C_s$ , not numbers.) If your calculation leads directly to a form that is already factored, you can leave that way — you do not need to expand out the polynomials.

Then calculate the numerical values of the poles. (And zeros, if there are any.)



$T(s) =$  \_\_\_\_\_

pole (and zero) values: \_\_\_\_\_

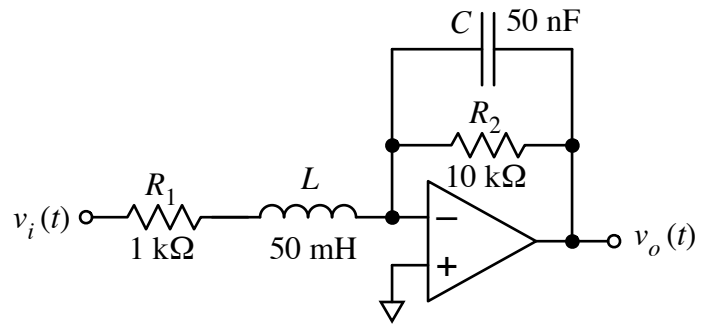

$T(s) =$  \_\_\_\_\_

pole (and zero) values: \_\_\_\_\_