

For the circuit shown at right, calculate  $v_{CE1}$  and  $v_{CE2}$ . Both BJTs have  $\beta_F = 100$ .

$v_{CE1} =$  \_\_\_\_\_

$v_{CE2} =$  \_\_\_\_\_

