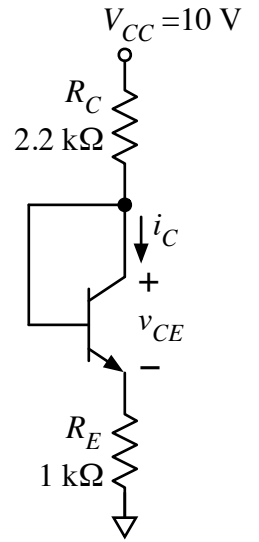


For the circuit shown, calculate i_C and v_{CE} . The BJT has $\beta_F = 100$. Note that the base is tied to the collector, $V_{BC} = 0$. This means something!

$i_C =$ _____

$v_{CE} =$ _____



For the circuit shown, determine the value of V_{BB} that will make $v_{CE1} = 3$ V. The BJTs both have $\beta_F = 100$.

$V_{BB} =$ _____

