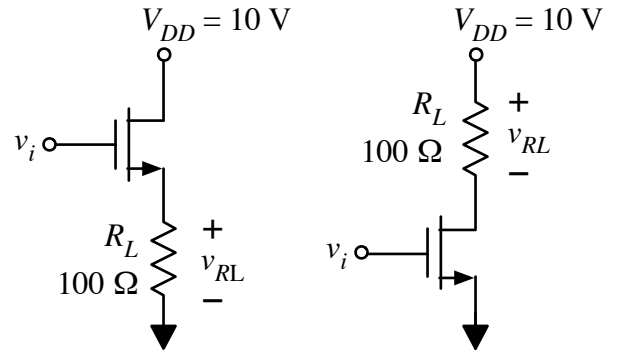


At right are two configurations for using an NMOS to deliver power to a load: one with the load connected to the source and one with the load connected to the drain.

Assume that the control voltage, v_i , is either 0 or 10 V. Of course, if $v_i = 0$ in either circuit, the NMOS is off and no current flows. For the case of $v_i = 10$ V for each circuit, calculate the load current i_{RL} and voltage, v_{RL} . Calculate the power delivered to the load. The calculate the power being delivered by the supply: $P_S = V_{DD} \cdot i_D$. Determine the power being dissipated in each of the transistors. What is the power delivery efficiency $\eta = P_{RL}/P_S$ in each case?



For the transistors, $K_n = 5 \text{ mA/V}^2$. and $V_T = 1 \text{ V}$.

$i_{RL} =$ _____

$i_{RL} =$ _____

$v_{RL} =$ _____

$v_{RL} =$ _____

$P_{RL} =$ _____

$P_{RL} =$ _____

$P_S =$ _____

$P_S =$ _____

$P_{NMOS} =$ _____

$P_{NMOS} =$ _____

$\eta =$ _____

$\eta =$ _____